

## Exercise 3

### Problem 3.1:

Simulate the PMOS current mirror circuit of Figure 3.1 using AIM-spice. Use geometry parameters  $W=20\ \mu\text{m}$  and  $L=2.0\ \mu\text{m}$  for both transistors, and the MOSFET model P1 that is described in the file 'modelcards\_v30.cir'.

- Set the bias current  $I_{bias} = 50\ \mu\text{A}$ ,  $V_{DD} = 1.7\ \text{V}$ ,  $R_L = 18\ \text{k}\Omega$ . How much is the current  $I_{out}$ ? How much is the output voltage  $V_{out}$ ? ( $I_{out} \approx 52\ \mu\text{A}$ ,  $V_{out} \approx 0.9\ \text{V}$ )
- Use the same parameter values as in a), but set now  $V_{DD} = 2.3\ \text{V}$ . How much are  $I_{out}$  and  $V_{out}$  now? ( $I_{out} \approx 56\ \mu\text{A}$ ,  $V_{out} \approx 1\ \text{V}$ )
- Use the same parameter values as in a), but set now  $R_L = 12\ \text{k}\Omega$  and  $V_{DD} = 1.7\ \text{V}$ . How much are  $I_{out}$  and  $V_{out}$  now? ( $I_{out} \approx 54\ \mu\text{A}$ ,  $V_{out} \approx 0.6\ \text{V}$ )
- Calculate the output impedance  $r_{out} = |\Delta V_{out}/\Delta I_{out}|$  of the current mirror circuit based on the results from a) and c) ( $r_{out} \approx 130\ \text{k}\Omega$ ). What is the Power Supply Rejection Ratio of this circuit (PSRR  $\approx 0.1$ )? PSRR is defined as  $\text{PSRR} = \Delta V_{out}/\Delta V_{DD}$ .

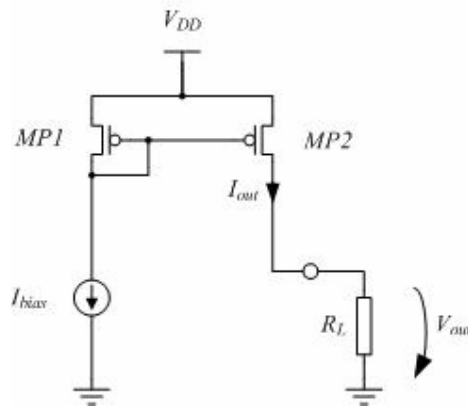


Figure 3.1

Problem 3.2:

Simulate the current mirror circuit of Figure 3.2 using AIM-spice. Use geometry parameters  $W=20\ \mu\text{m}$  and  $L=2.0\ \mu\text{m}$  for all the four transistors, and the MOSFET model P1 that is described in the file 'modelcards\_v30.cir'.

- Set the bias current  $I_{bias} = 50\ \mu\text{A}$ ,  $V_{DD} = 2.0\ \text{V}$ ,  $R_L = 18\ \text{k}\Omega$ . How much are  $I_{out}$  and  $V_{out}$ ? ( $I_{out} \approx 50\ \mu\text{A}$ ,  $V_{out} \approx 0.9\ \text{V}$ )
- Use the same parameter values as in a), but set now  $V_{DD} = 2.3\ \text{V}$ . How much are  $I_{out}$  and  $V_{out}$  now? ( $I_{out} \approx 50\ \mu\text{A}$ ,  $V_{out} \approx 0.9\ \text{V}$ )
- Use the same parameter values as in a), but set now  $R_L = 12\ \text{k}\Omega$  and  $V_{DD} = 2.0\ \text{V}$ . How much are  $I_{out}$  and  $V_{out}$  now? ( $I_{out} \approx 50\ \mu\text{A}$ ,  $V_{out} \approx 0.6\ \text{V}$ )
- What is the output impedance  $r_{out}$  of this circuit? ( $r_{out} \approx 6\ \text{M}\Omega$ )  
 What is the PSRR of this circuit? (PSRR < 0.01)  
 Compare the results in this problem with the results of Problem 3.1.

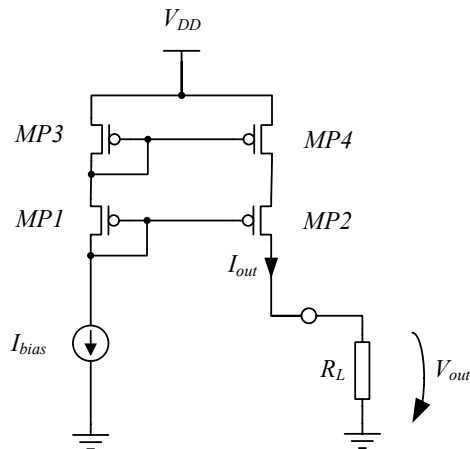


Figure 3.2

Problem 3.3:

The source follower circuit of Figure 3.3 has the following parameters:

$$W/L = 100 \mu\text{m}/1.6 \mu\text{m}$$

$$\mu_n C_{ox} = 90 \mu\text{A}/\text{V}^2$$

$$\mu_p C_{ox} = 30 \mu\text{A}/\text{V}^2$$

$$I_{bias} = 100 \mu\text{A}$$

$$\gamma_n = 0.5 \text{ V}^{1/2}$$

$$r_{ds-n} (\Omega) = 8000L(\mu\text{m})/I_D(\text{mA})$$

$$V_{SB} = 2 \text{ V}$$

$$R_{in} = 180 \text{ k}\Omega$$

$$C_L = 0.5 \text{ pF}$$

$$C_{gs1} = 0.2 \text{ pF}$$

$$C_{gd1} = 15 \text{ fF}$$

$$C_{sb1} = 40 \text{ fF}$$

$$C_{in} = 30 \text{ fF}$$

- Find the output impedance of the source follower at low frequencies.
- Find the voltage gain of the circuit at low frequencies.

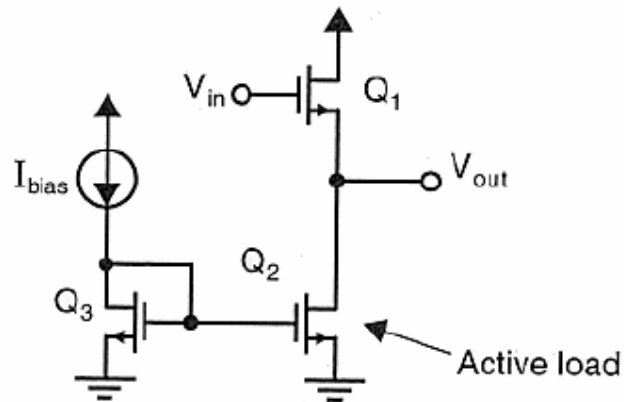


Figure 3.3