

## TFE 4200 Analog Integrated Circuits

### Problem sheet #5

#1. Consider a feedback amplifier for which the open-loop transfer function  $A(s)$  is given by

$$A(s) = \left( \frac{10}{1 + s/10^4} \right)^3$$

Let the feedback factor  $\beta$  be a constant and independent of frequency. Find the frequency  $\omega_{180}$  at which the phase of the loop transfer function ( $A(s)\beta$ ) is  $-180^\circ$ . Then, show that the feedback amplifier will be stable if the feedback factor  $\beta$  is less than a critical value  $\beta_{cr}$  and unstable if  $\beta$  is greater than or equal to  $\beta_{cr}$ , and find the value of  $\beta_{cr}$ .

#2. An op amp having a single-pole rolloff at 100 Hz and a low-frequency gain of  $10^5$  is operated in a feedback loop with  $\beta=0.01$ . What is the factor by which feedback shifts the pole? To what frequency? If  $\beta$  is changed to a value that results in a closed-loop gain of  $+1$ , to what frequency does the pole shift?

#3. An amplifier with a low-frequency gain of 100 and poles at  $10^4$  rad/s and  $10^6$  rad/s is incorporated in a negative-feedback loop with feedback factor  $\beta$ . For what values of  $\beta$  do the poles of the closed-loop amplifier coincide? What is the corresponding  $Q$  of the resulting second-order system? For what value of  $\beta$  is a maximally flat response achieved? What is the low-frequency closed-loop gain in the maximally flat case?

#4. Consider an op amp having a single-pole open-loop response with  $A_0 = 10^5$  and  $f_p = 10$  Hz. Let the op amp be ideal (infinite input impedance, zero output impedance). If this amplifier is connected in the noninverting configuration with a nominal low-frequency closed-loop gain of 100, find the frequency at which  $|A\beta| = 1$ . Also, find the phase margin.

#5. Find the closed-loop gain at  $\omega_1$  (the frequency at which magnitude of loop gain is unity) relative to the low-frequency gain ( $1/\beta$ ) when the phase margin is  $30^\circ$ ,  $60^\circ$  and  $90^\circ$ .

#6. Consider an op amp whose open-loop gain is identical to that of the one shown in Fig.1. Assume that the op amp is ideal and it is connected as a differentiator. Show that for stable performance the differentiator time constant should be greater than 159 ms.

**HINT:** For stable performance "at the intersection of  $20\log(1/|\beta[j\omega]|)$  and  $20\log|A[j\omega]|$  the difference of slopes should not exceed 20 dB/decade"

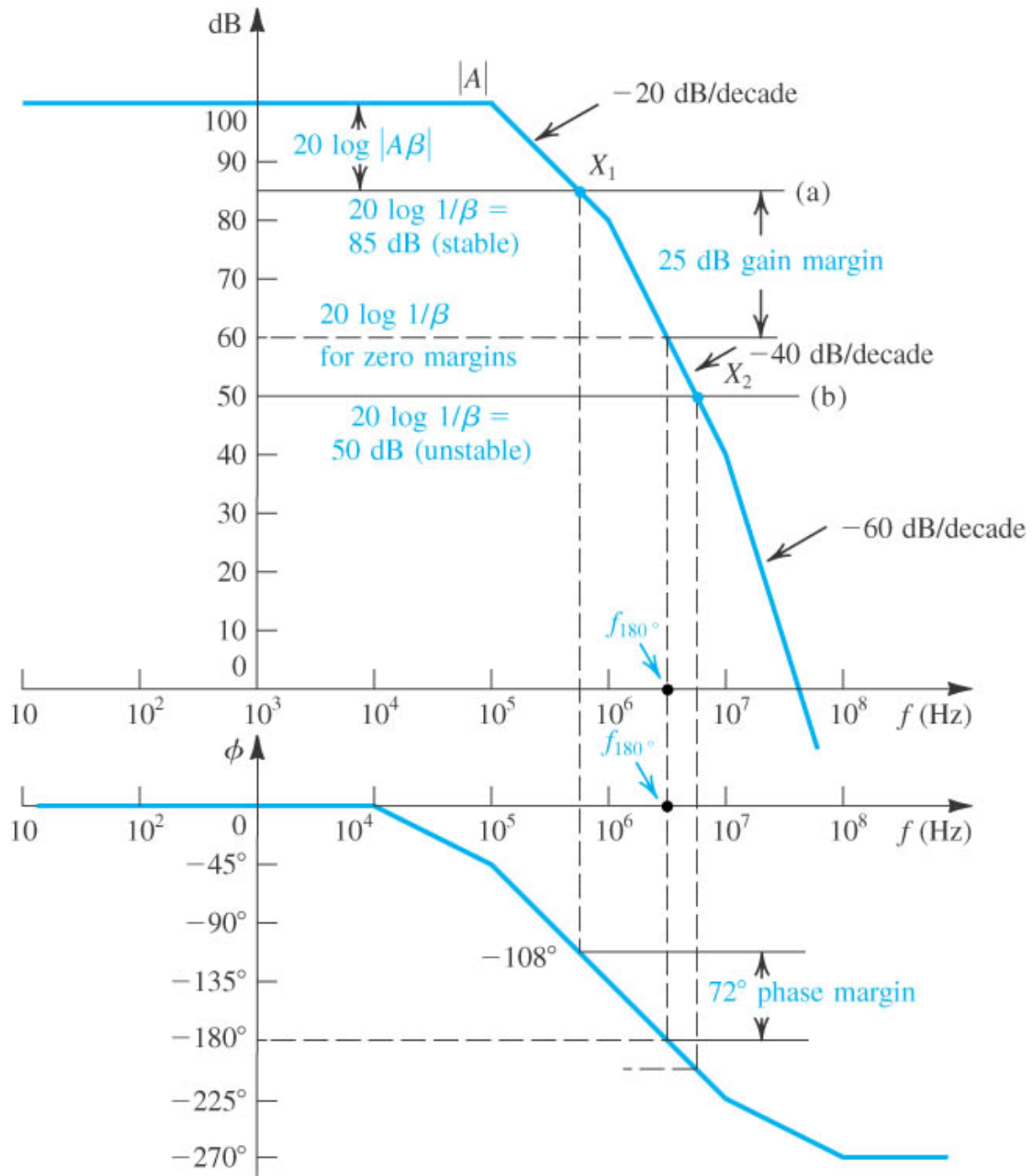


Fig. 1.