

## TFE 4200 Analog Integrated Circuits Problem sheet #6

1. Design an inverting amplifier (see Fig. 1) having a gain of -10 and an input resistance of 100 k $\Omega$ . [Give the values of R<sub>1</sub> and R<sub>2</sub>.]

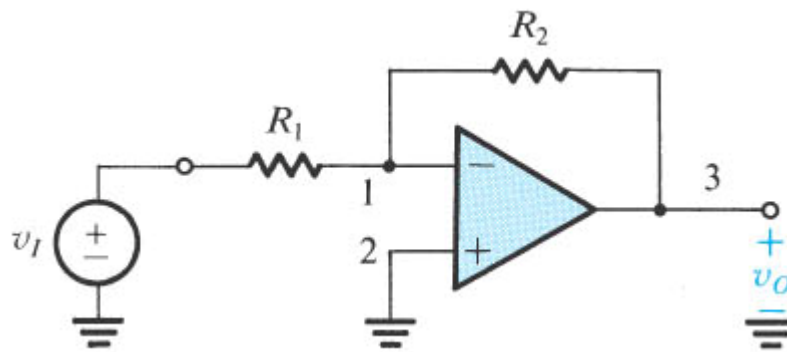


Fig. 1

2. The circuit shown in Fig. 2(a) can be used to implement a transresistance amplifier. Find the value of the input resistance  $R_i$ , the transresistance  $R_m$ , and the output resistance  $R_o$  of the transresistance amplifier. If the signal source shown in Fig. 2(b) is connected to the input of the transresistance amplifier, find its output voltage.

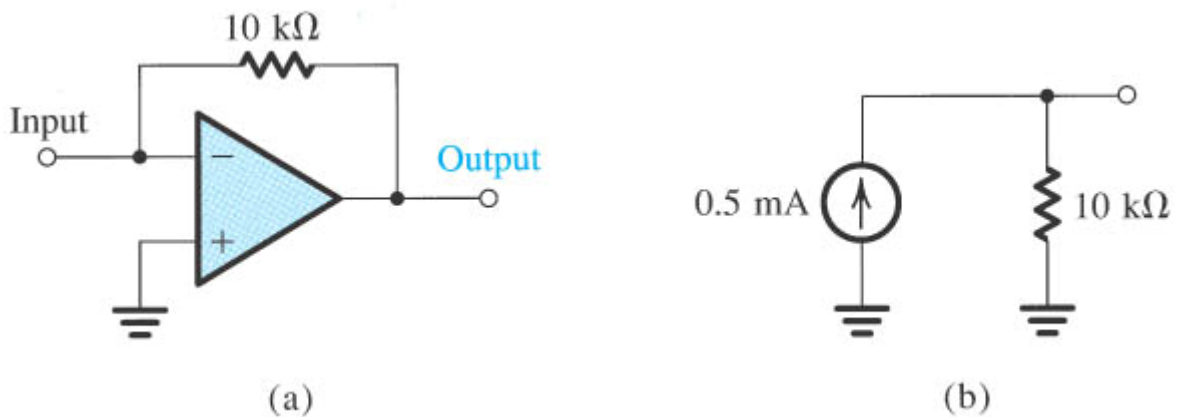


Fig. 2

3. An internally compensated op amp is specified to have an open-loop dc gain of 106 dB and a unity gain frequency of 3 MHz. Find  $f_{3dB}$  and the open-loop gain (in dB) at  $f_{3dB}$ . Also, find the open-loop dc gain at 300 Hz, 3 kHz, 12 kHz, and 60 kHz.
4. An op amp having a 106-dB gain at dc and a single-pole frequency response with  $f_t = 2$  MHz is used to design a noninverting amplifier with nominal dc gain of 100. Find the 3-dB frequency of the closed-loop gain.